

ZVxPlus Application

PA Design



Introduction

- The power amplifier
- Figures of merit
- Concept of load line
- Tuning in Practice: Source and load pull
- Classes of operations
- Conclusion

The power amplifier

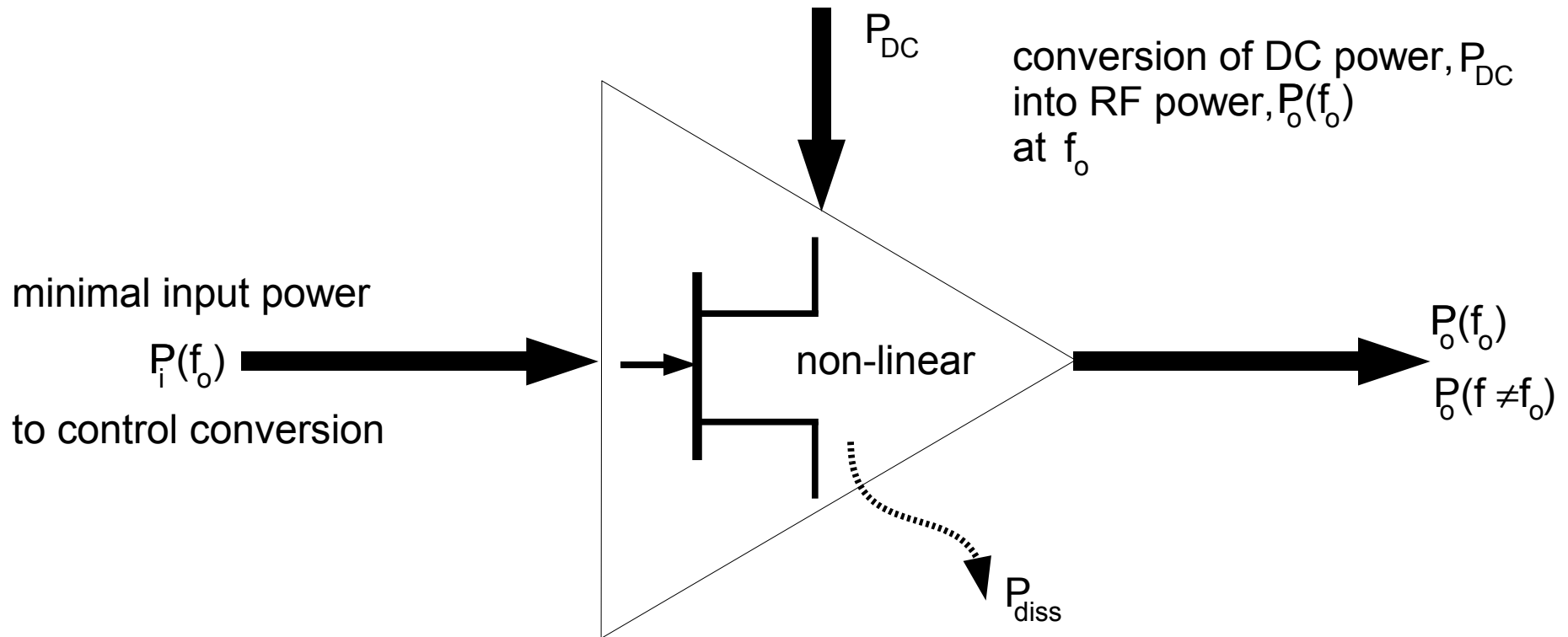


Figure of merit

- Efficiency: quality factor for DC consumption

$$\eta = \frac{P_o(f_o)}{P_i(f_o) + P_{DC}}$$

- Power Added Efficiency (PAE): ratio between the RF power 'added' by the amplifier and the DC power required for this addition.



$$PAE = \frac{P_o - P_i}{P_{DC}}$$

linearity: Class A: excellent
Class AB: between A and B
Class B: moderate
Class C: poor


η : Class A: 50%
Class AB: between A and B
Class B: 78.5%
Class C: >78.5%

Concept of load line

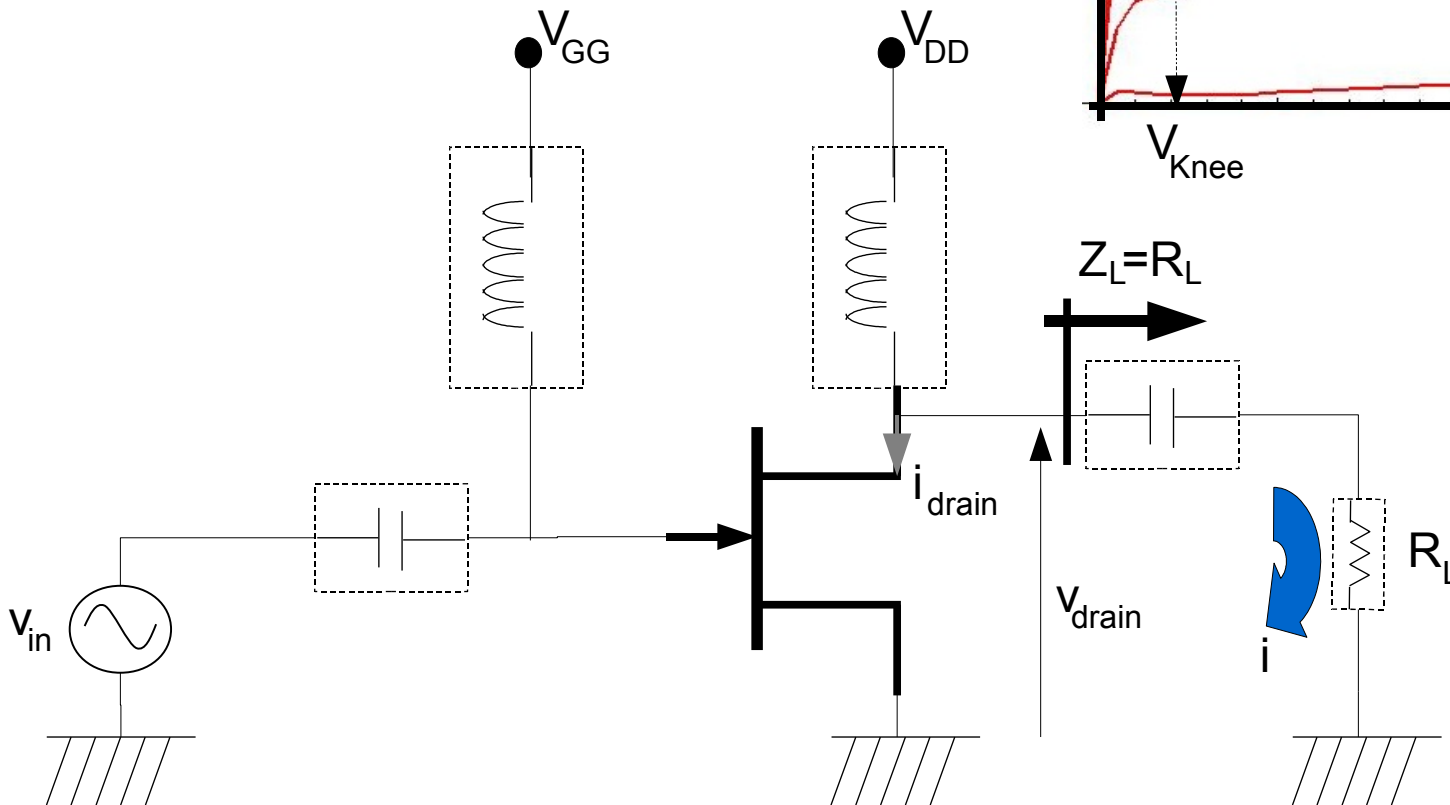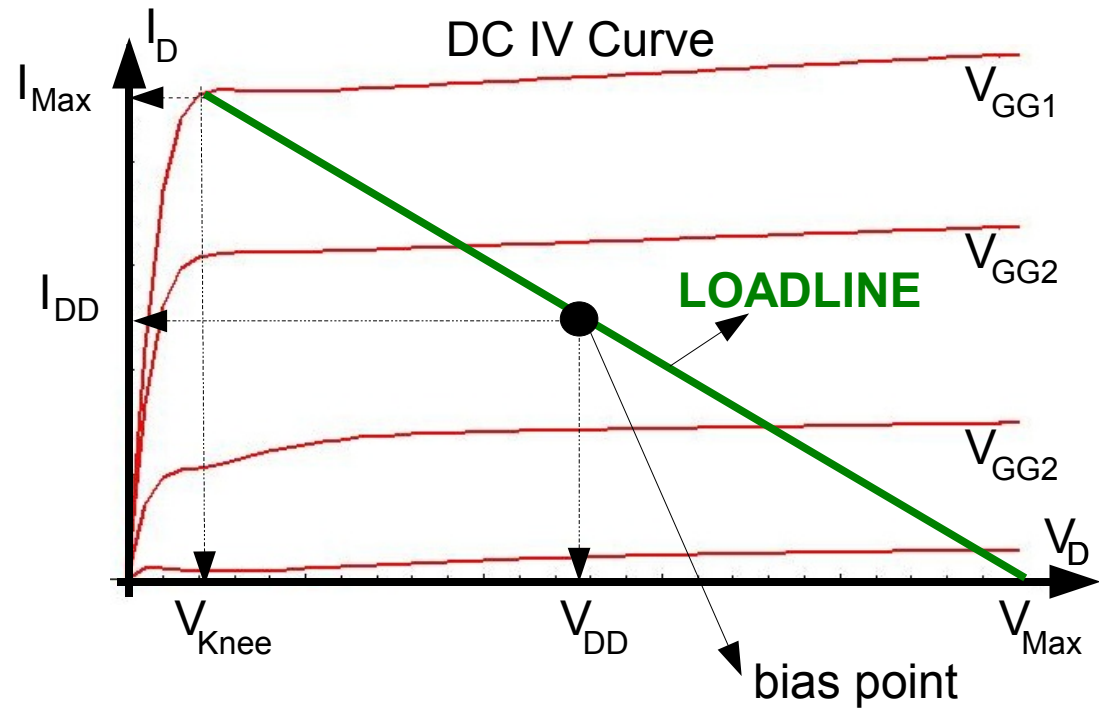
$$R_L = \frac{V_{Max} - V_{Knee}}{I_{Max}}$$



Classic Source / load pull

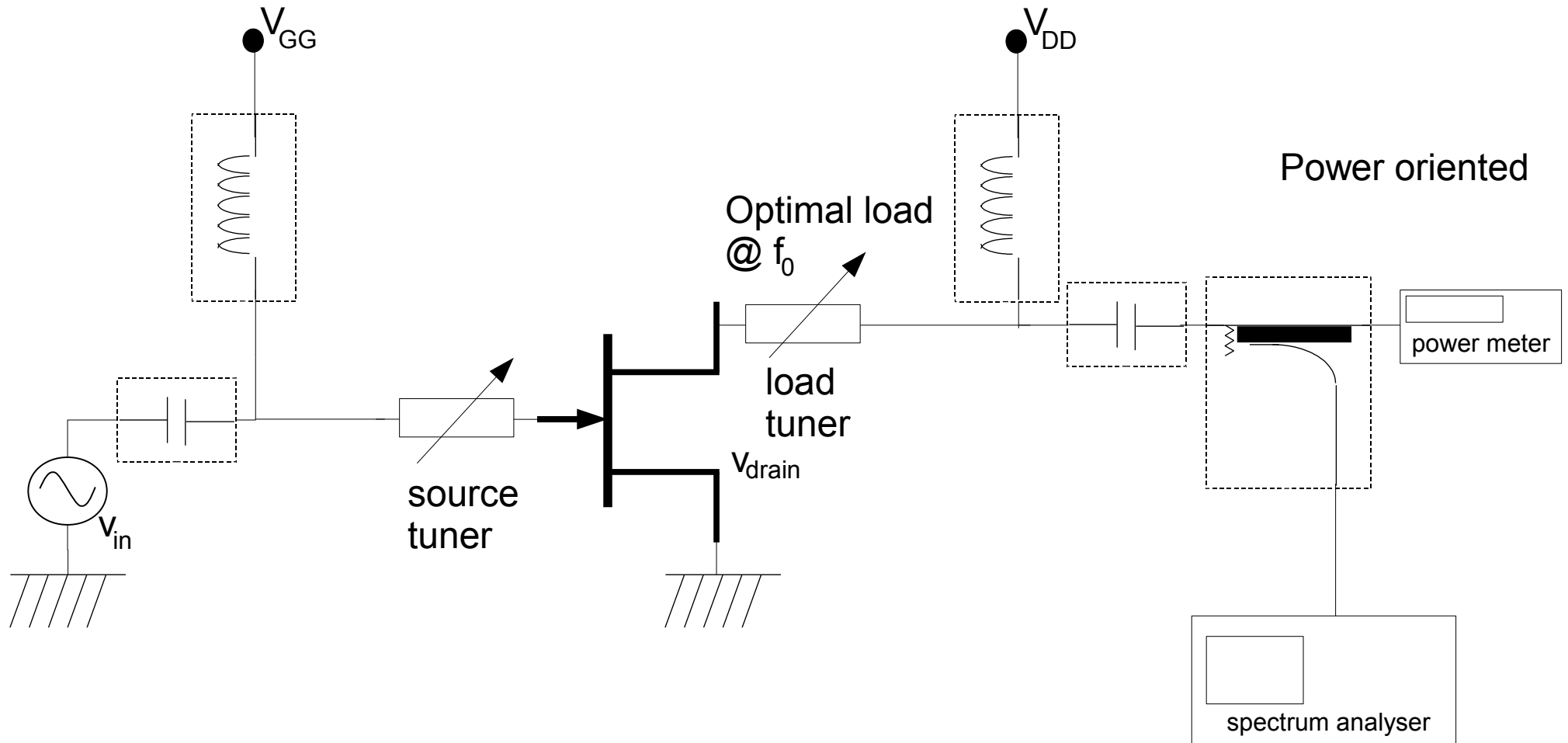

Source / load pull with the ZVxPlus

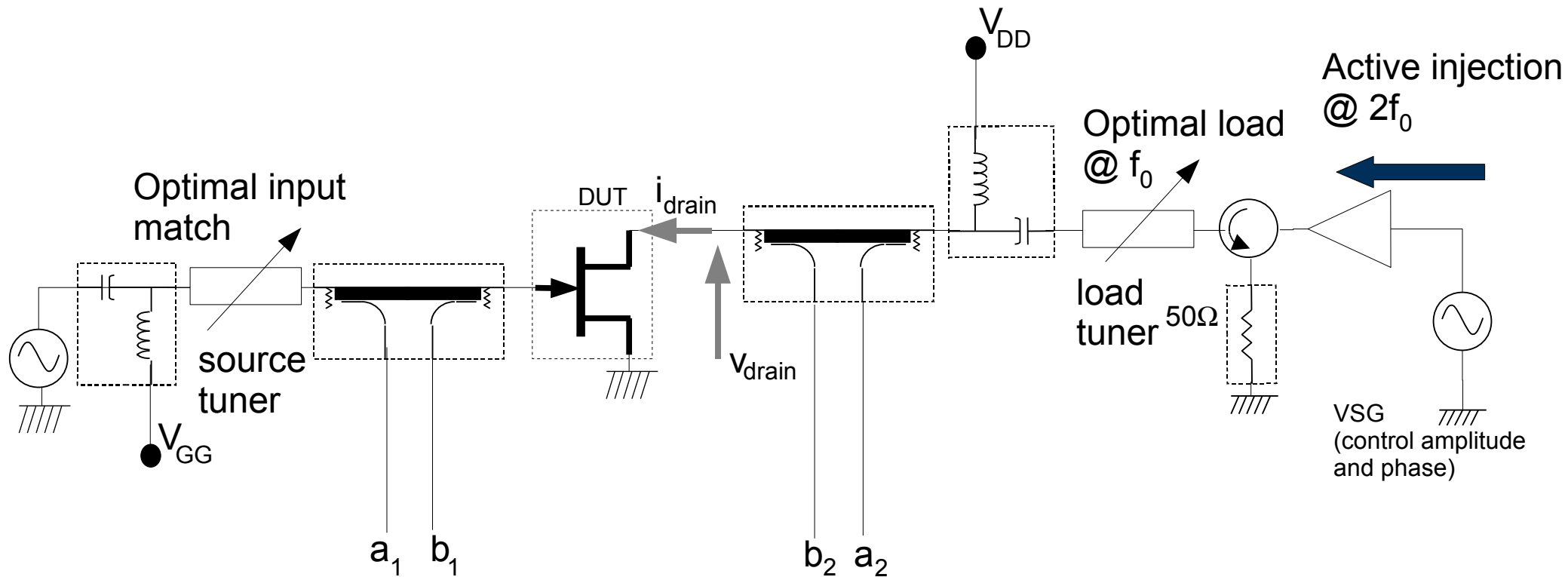

No power meter needed
No spectrum analyser needed

→ This can be done using the ZVxPlus
and we get the waveforms for free

Classes of operation



- Classes of operations

- Class A
- Class AB
- Class B

→ Loadline?



→ Drain current and drain voltage waveforms?

Classes of operation: Class A

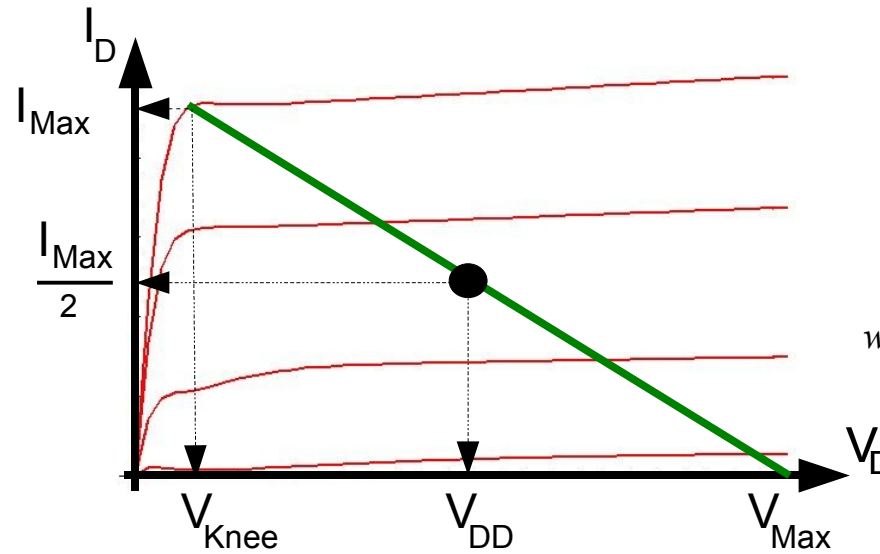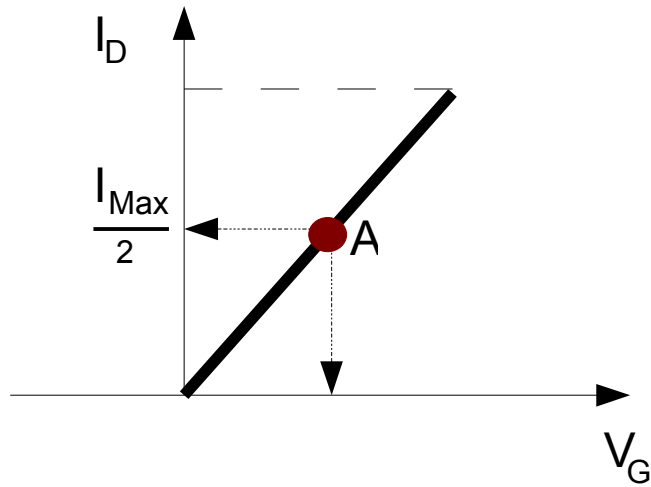


theoretical
 $\eta = 50\%$
 if $V_{Knee} = 0V$

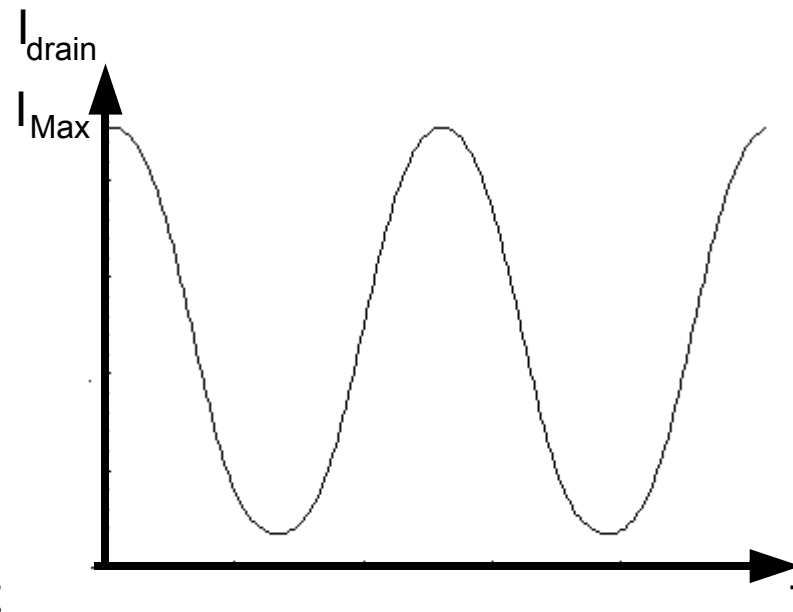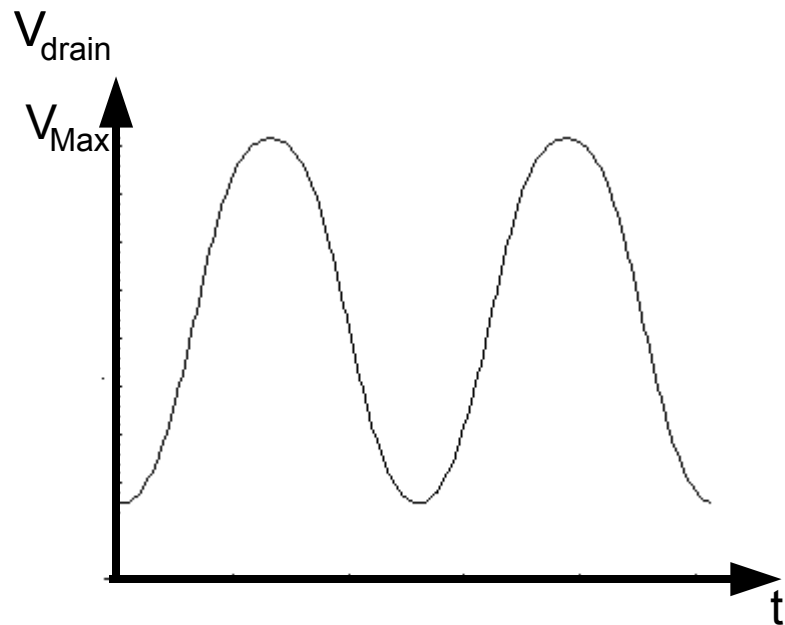
$$R_L = \frac{V_{DD}}{0.5 I_{Max}}$$
 with $V_{DD} \approx \frac{V_{Max} - V_{Knee}}{2} + V_{Knee}$



Fundamental load tuning

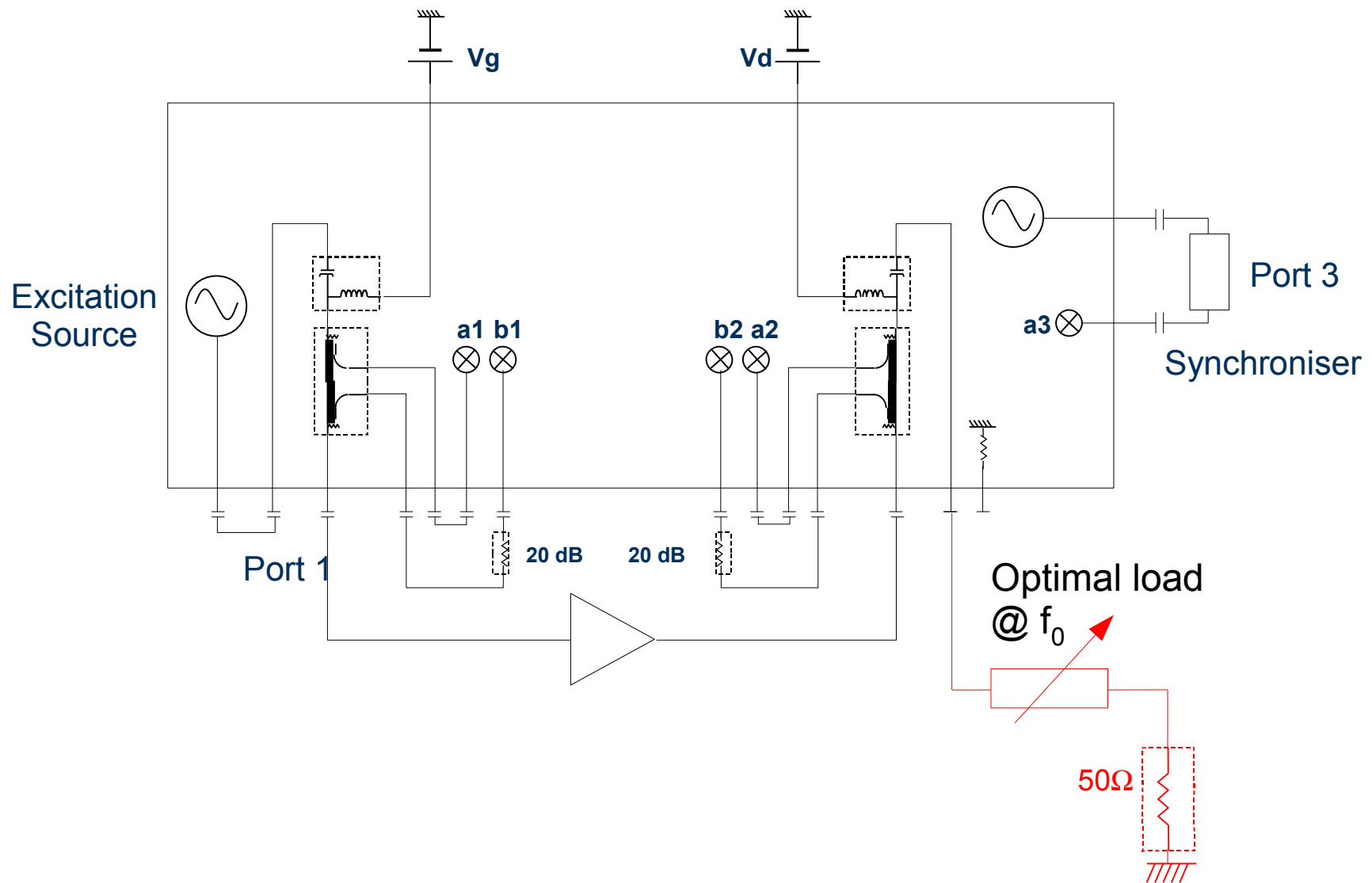


Class A in practice: Overrange

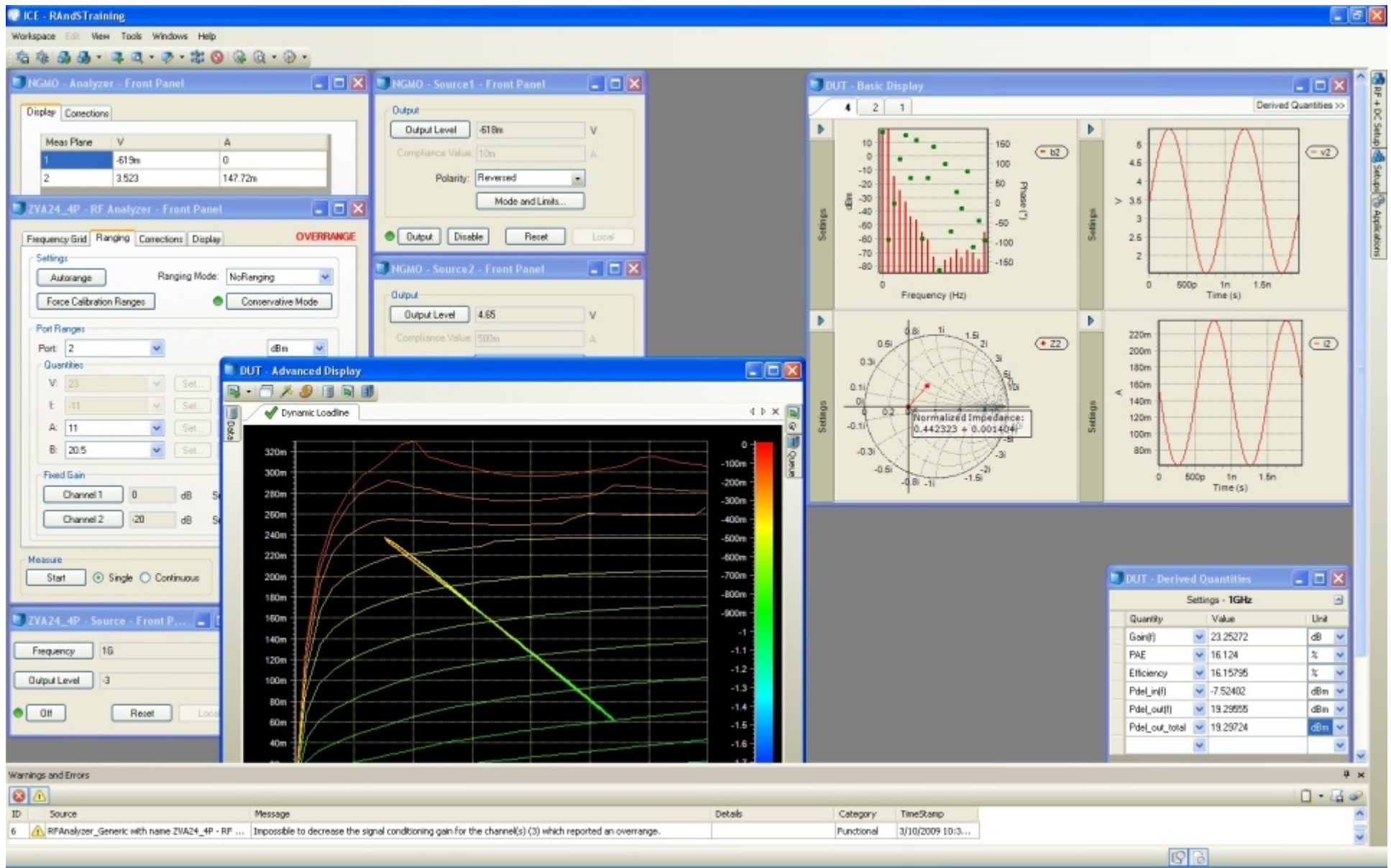


Ovrange Solution




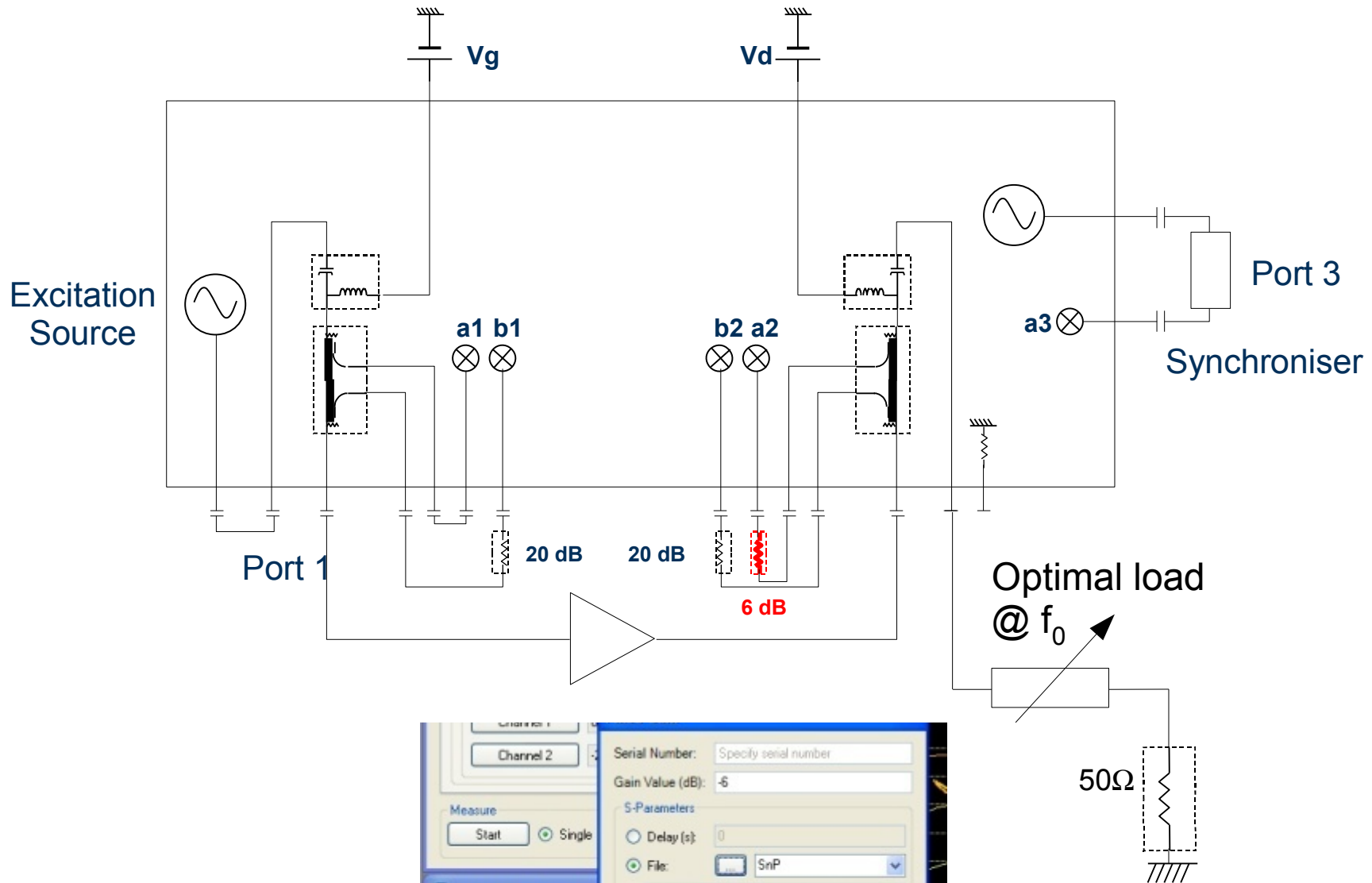
Adding a characterised 6dB attenuator in a2 channel **on the fly!**



Class A in practice

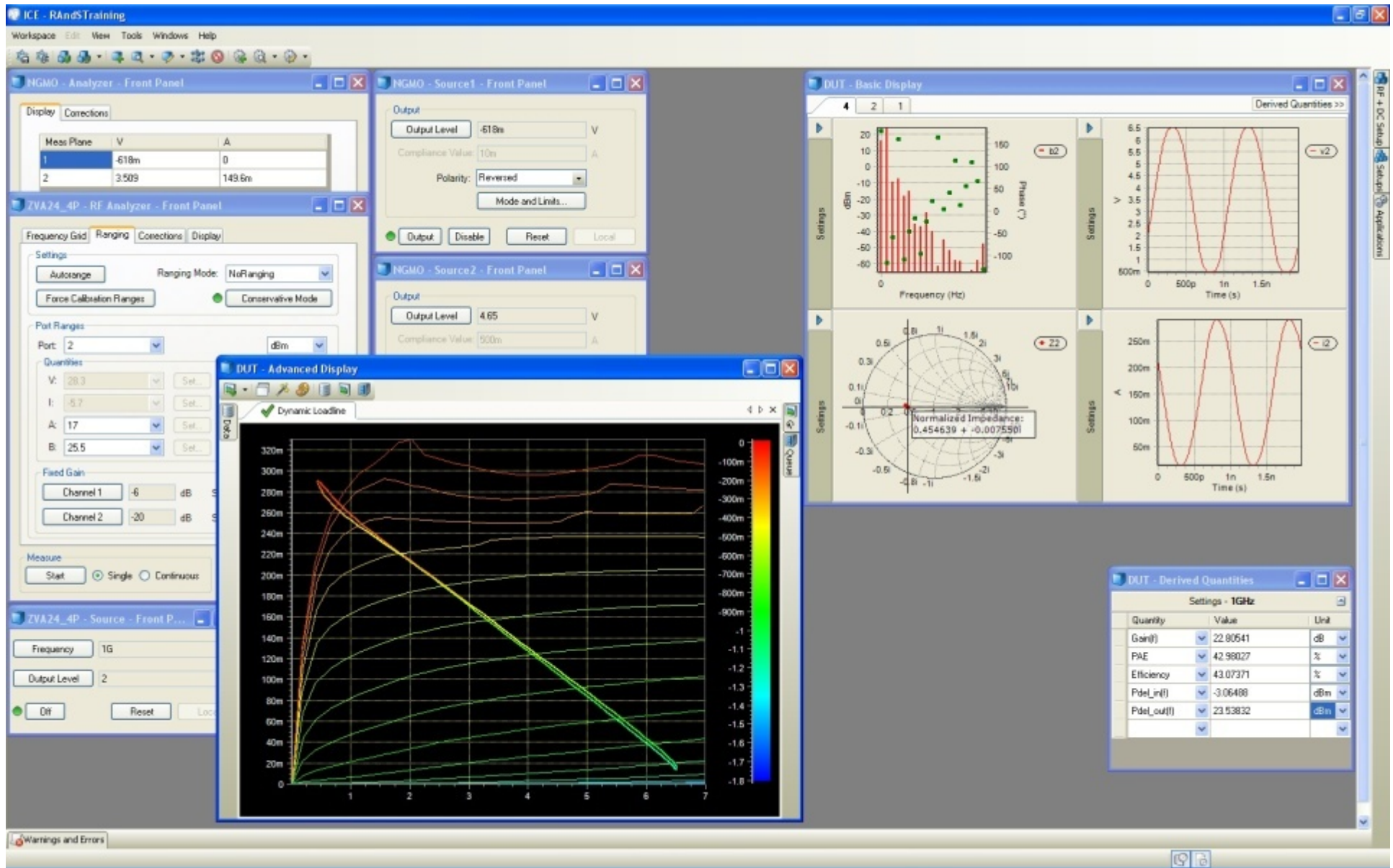


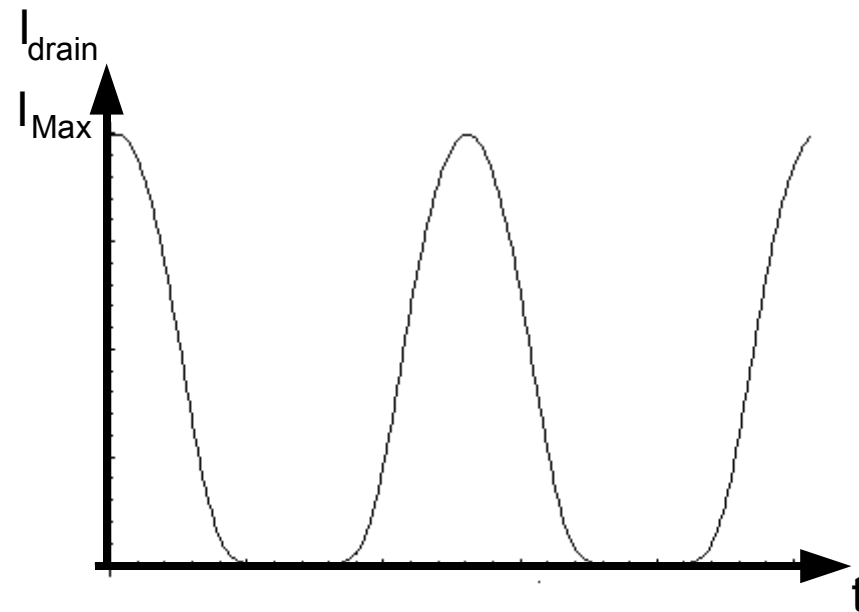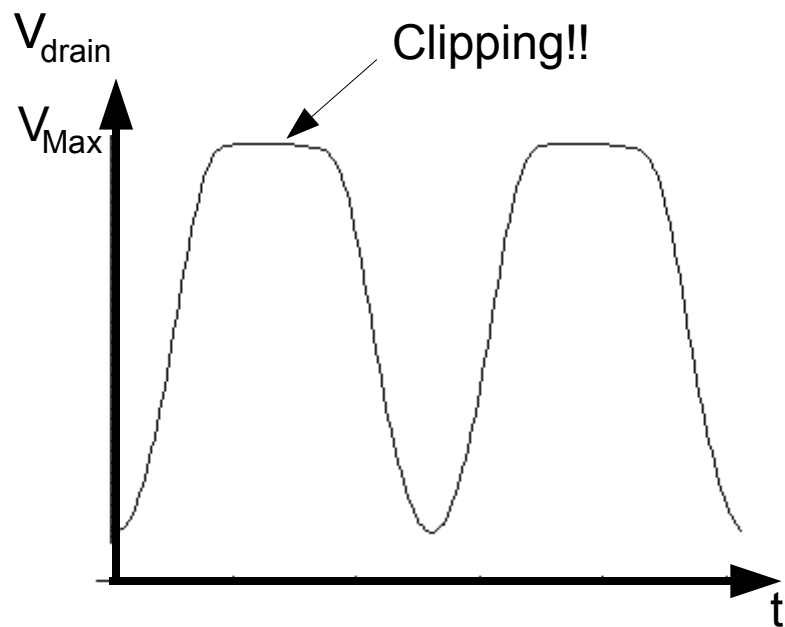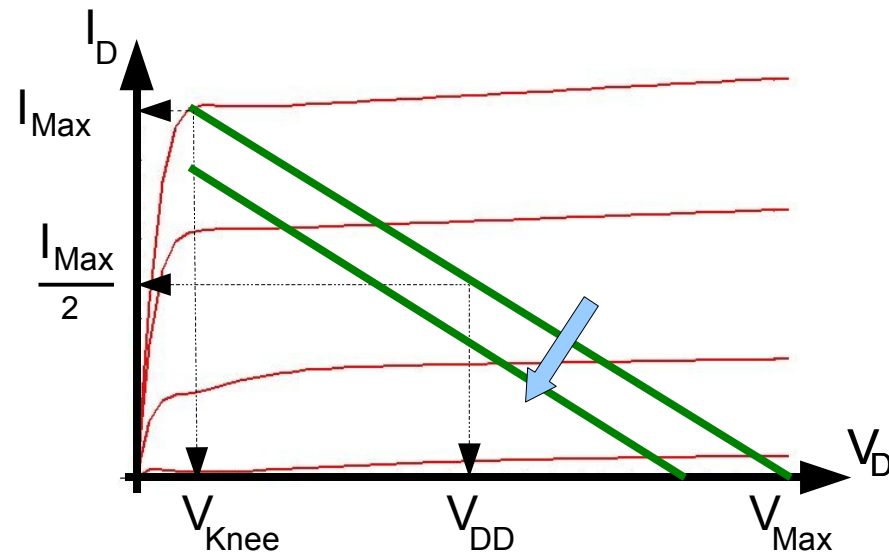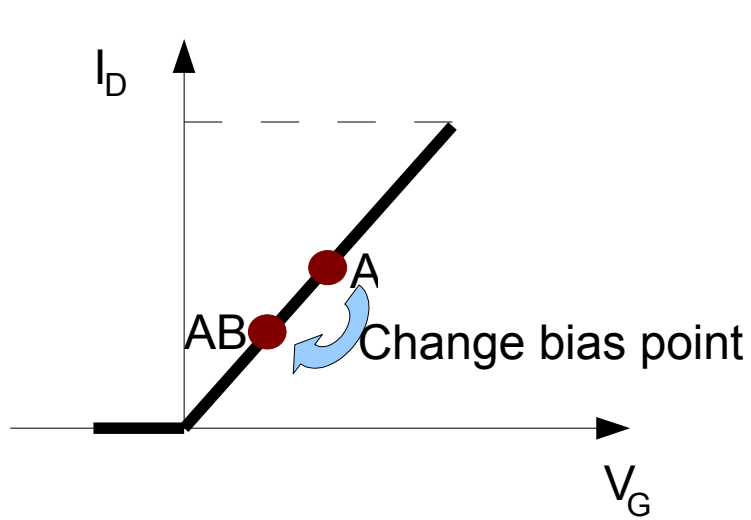Classes of operation: From Class A to AB, the first step




The drain voltage contains harmonics → goal is a sine wave drain voltage

Class AB, first step in Practice

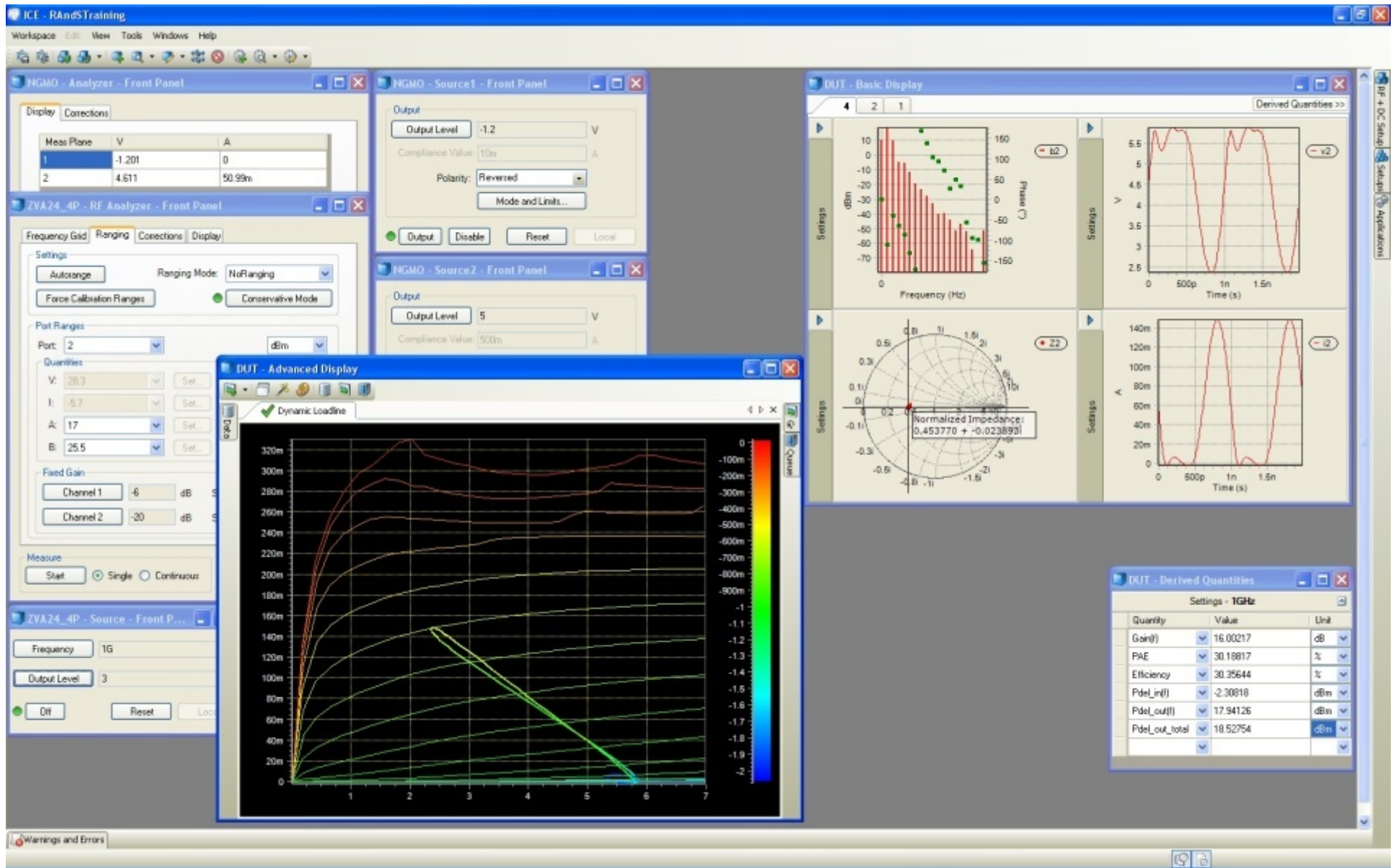

Harmonic output termination: tuned load

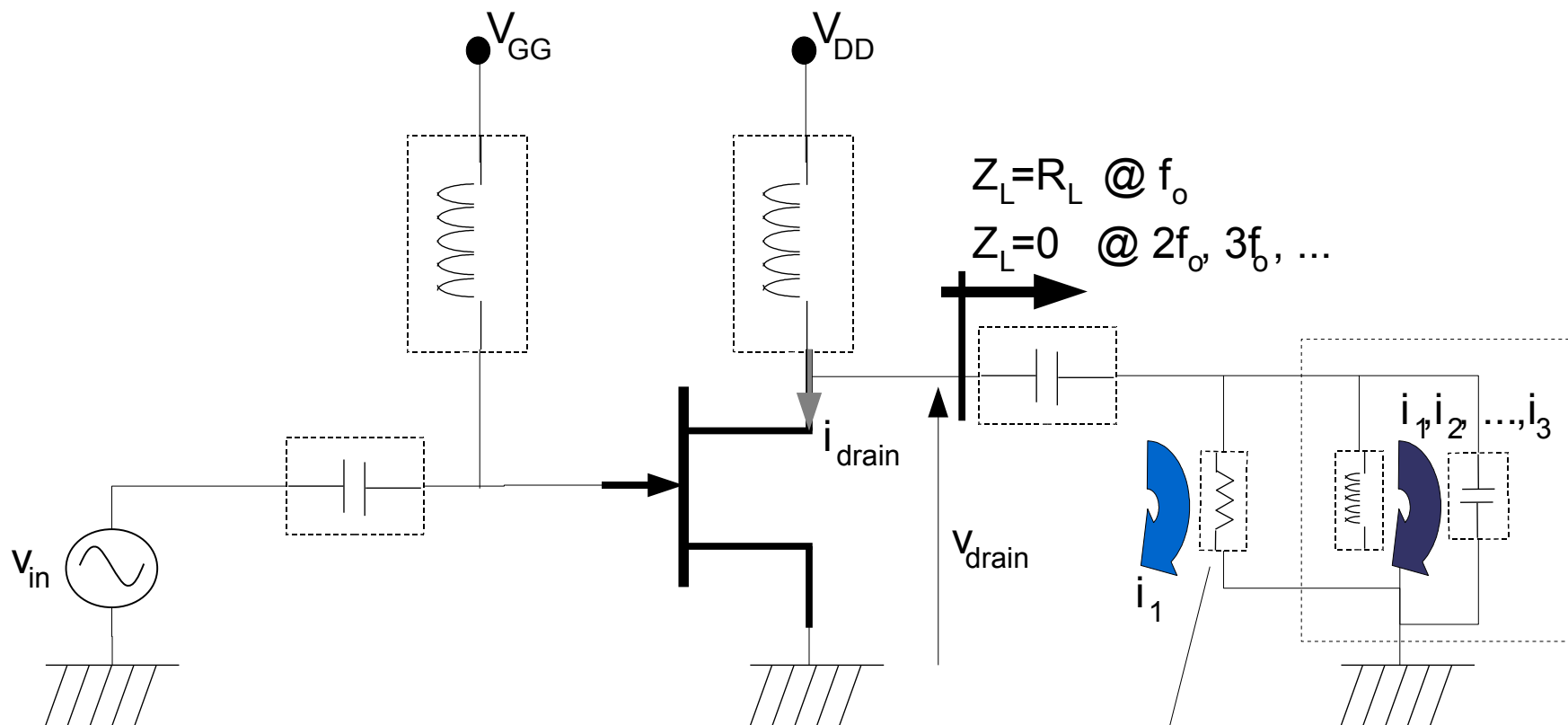



In case of :

- a perfect harmonic short
- maximum voltage swing of $2V_{DD}$
- no knee region

the optimum value of load resistance will be:

$$R_L = \frac{V_{DD}}{I_{@f_0}}$$



Classes of operation: Class AB

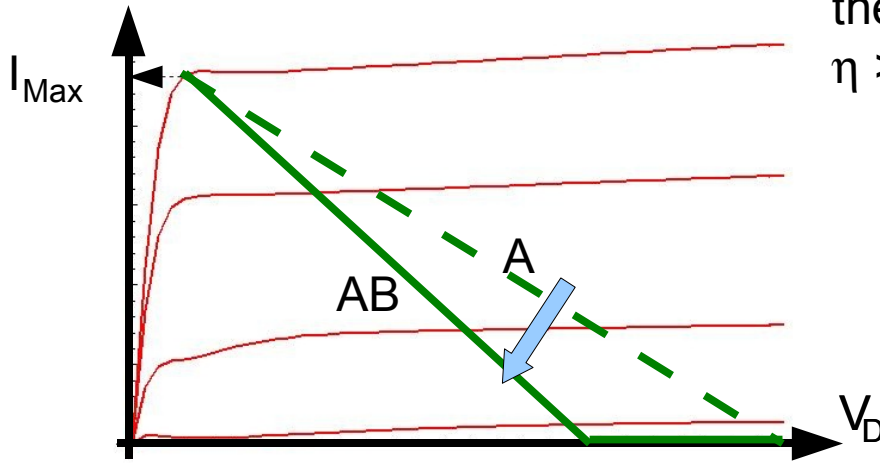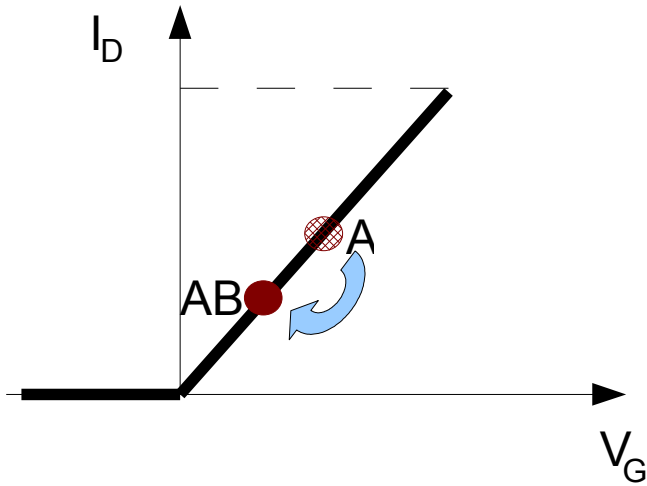


theoretical
 $\eta > 50\%$ and $< 78.5\%$

due to:

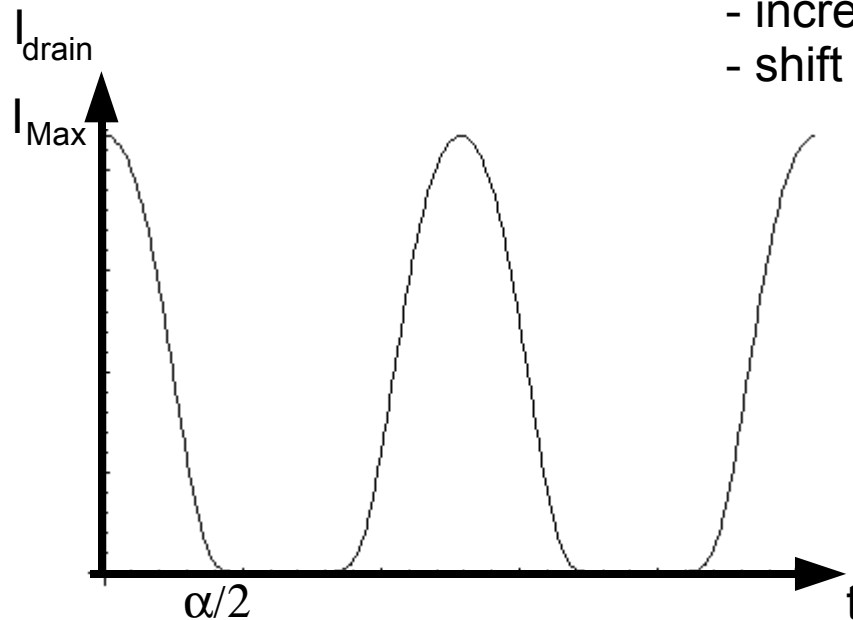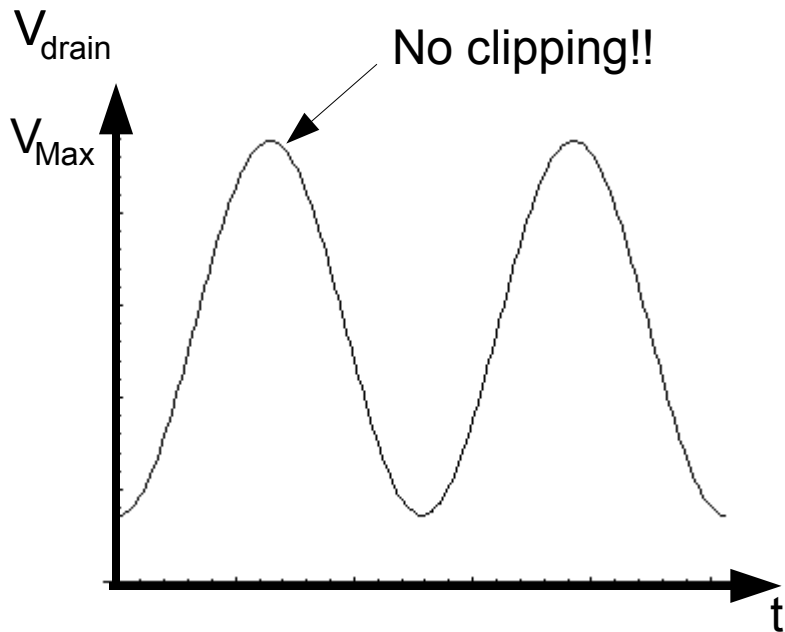
- termination at harmonics
- increased input signal
- shift of V





Harmonic active tuning

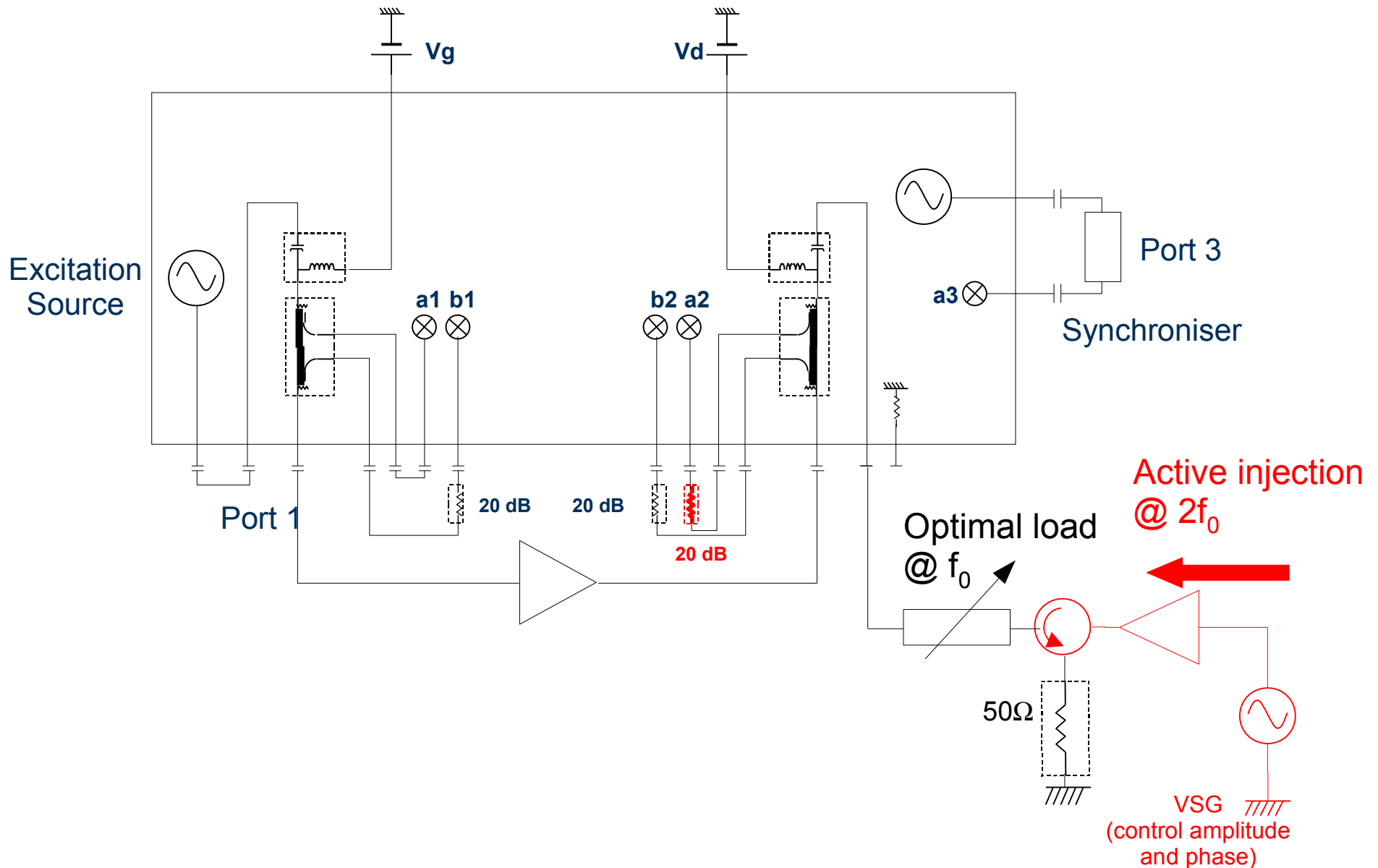



Class AB in practice

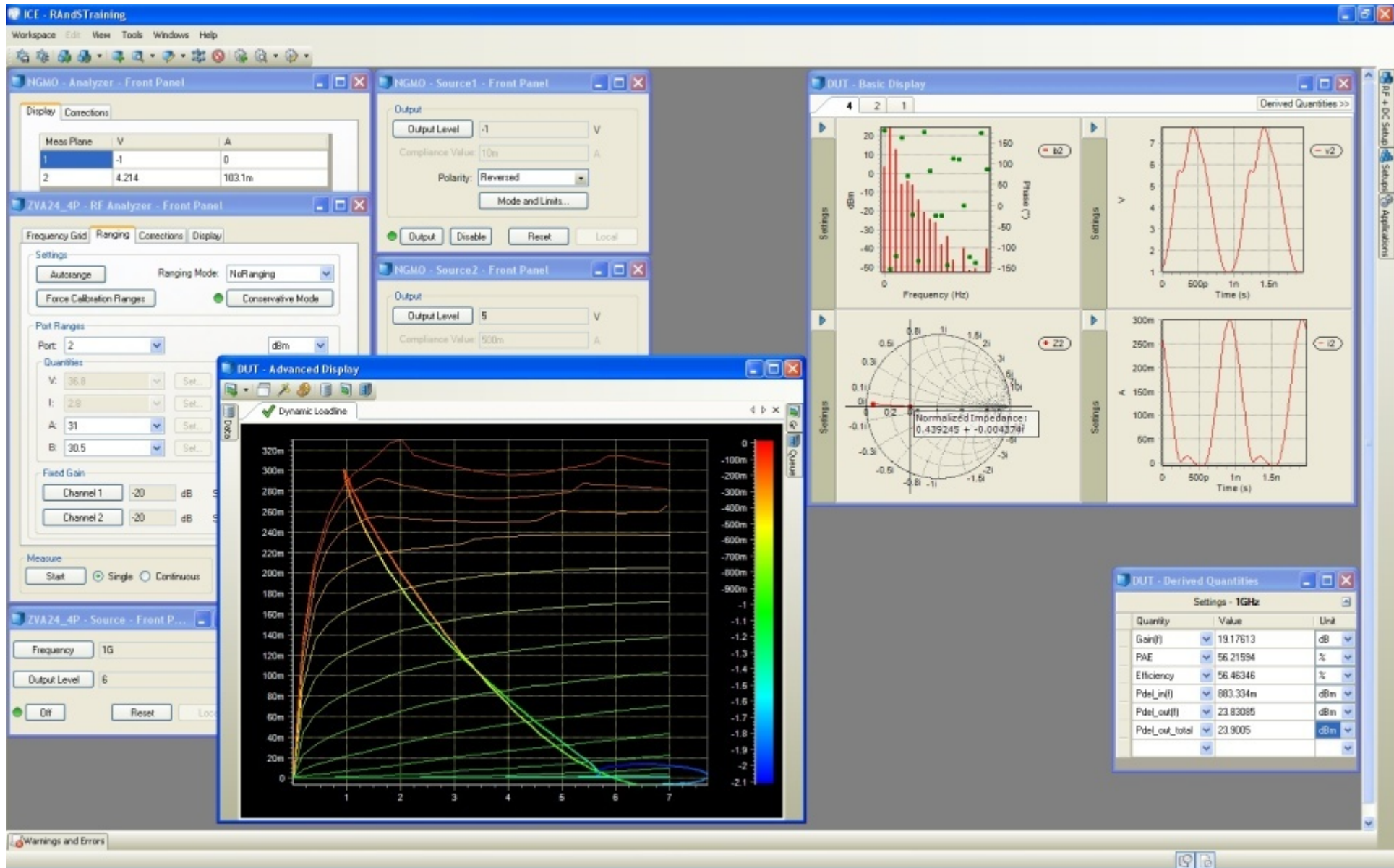

Classes of operation: Class B

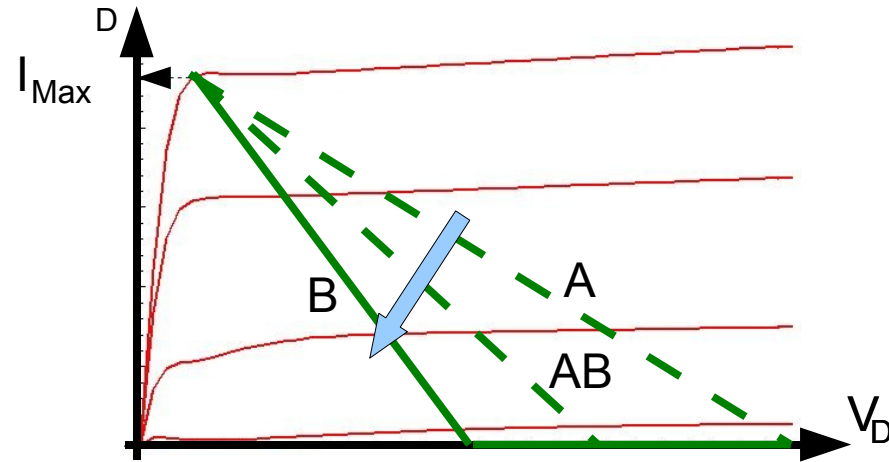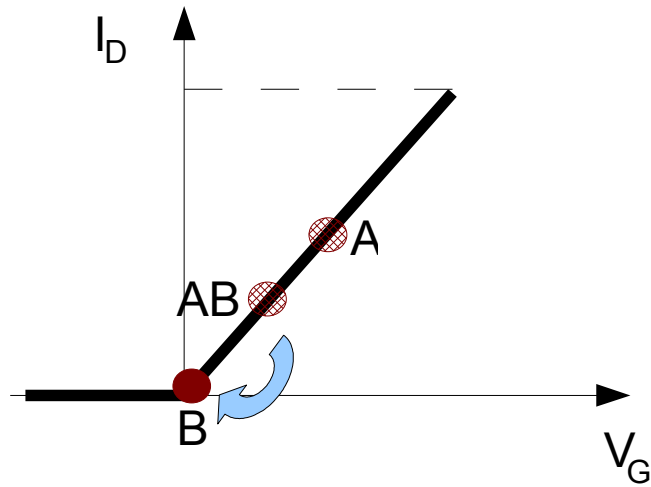


theoretical
 $\eta=78.5\%$

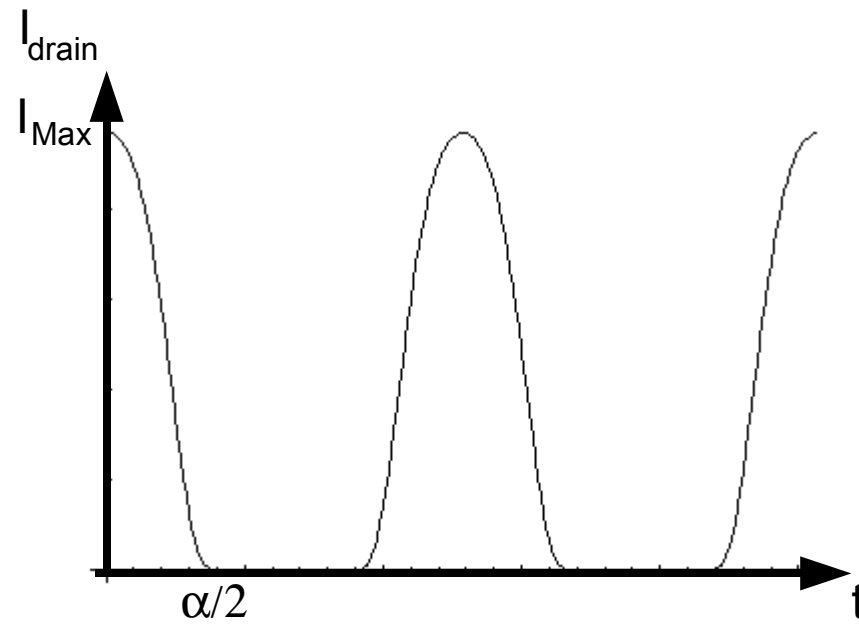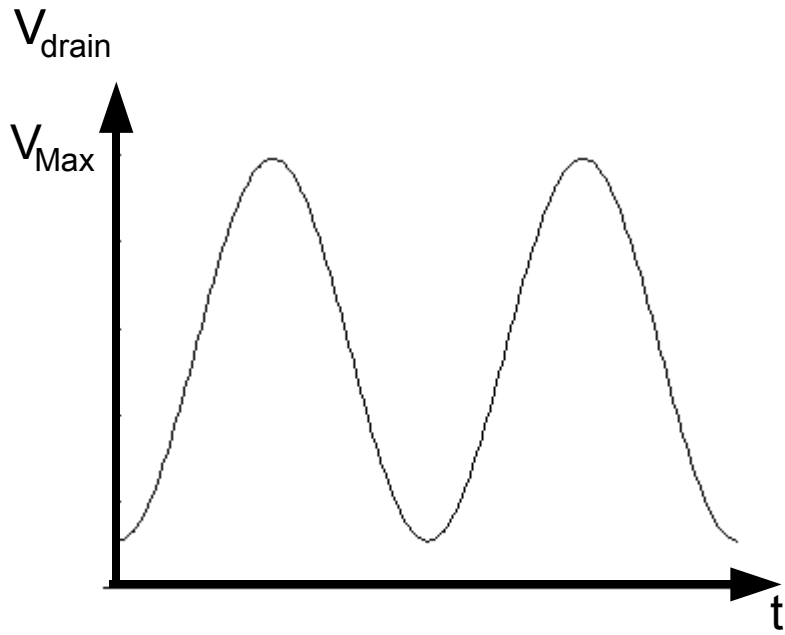

Note: in case of a perfect short at all harmonics

... to Class B

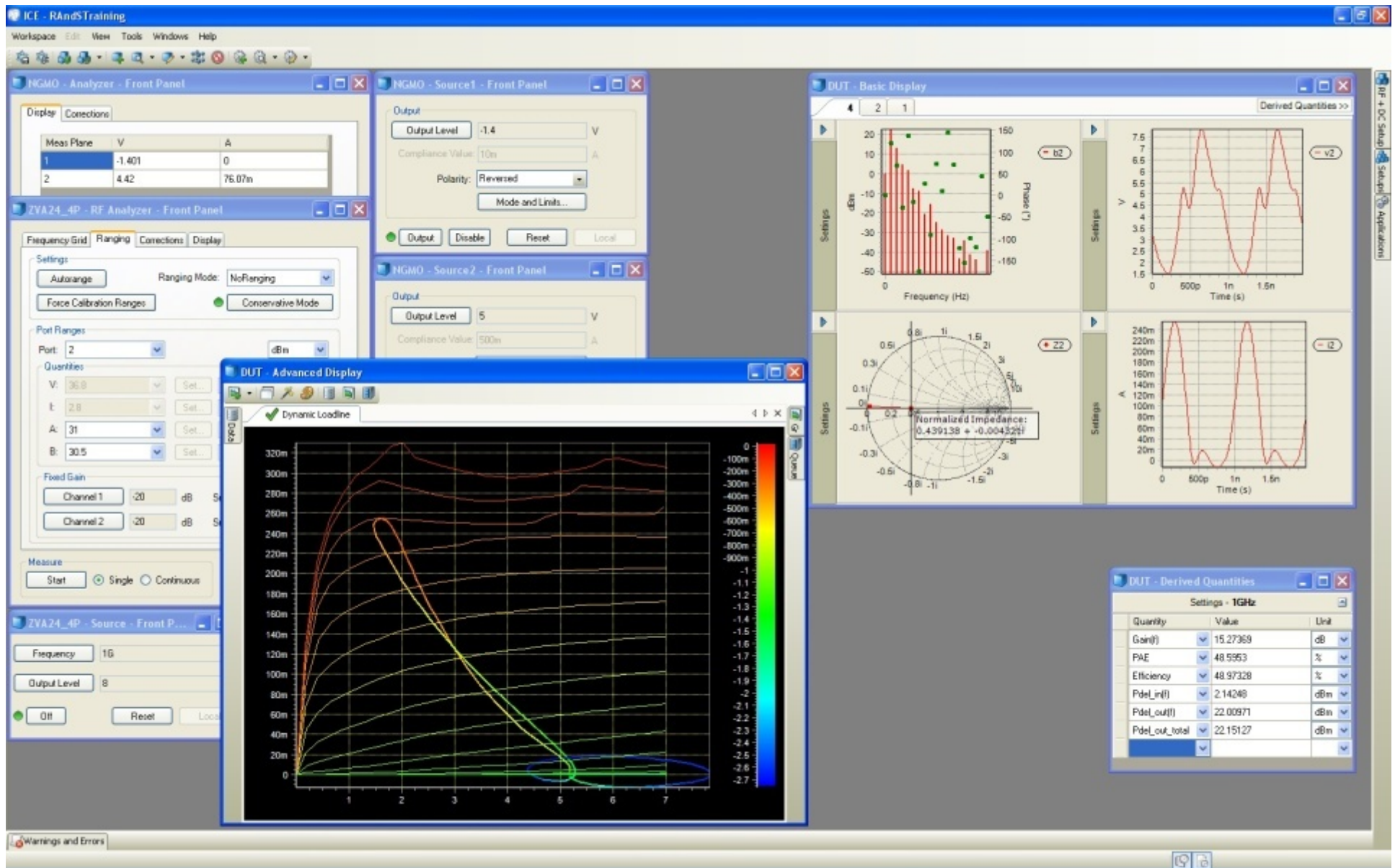

Conclusion

- Fast Power Amplifier Design using ZVxPlus has been demonstrated.
- Using the ZVxPlus, a RF Design engineer can do **on the fly** a concrete application design, with one single tool. This tool gives all the information needed for the design.

It will surely open new domains and applications.

For more information

info@nmdg.be

www.nmdg.be